

AUSTRALIAN NATIONAL UNIVERSITY
Department of Engineering

ENGN 2211 Electronic Circuits and Devices
 Problem Set #8 BJT CE Amplifier Circuits

Q1

Consider the common-emitter BJT amplifier circuit shown in Figure 1.

Assume $V_{CC} = 15\text{ V}$, $\beta = 150$, $V_{BE} = 0.7\text{ V}$,
 $R_E = 1\text{ k}\Omega$, $R_C = 4.7\text{ k}\Omega$, $R_1 = 47\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, $R_L = 47\text{ k}\Omega$, $R_s = 100\text{ }\Omega$.

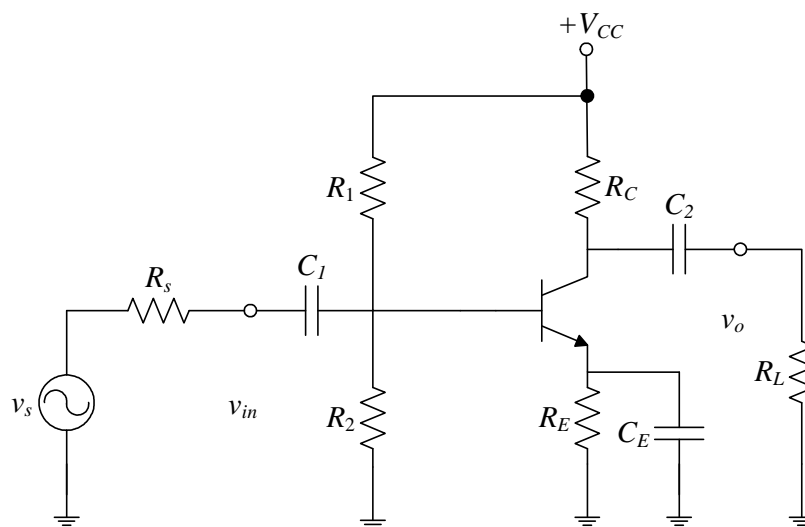


Figure 1: The circuit for Question 1.

- Determine the Q-point.
- Sketch the DC load-line. What is the maximum (peak to peak) output voltage swing available in this amplifier.
- Draw the AC equivalent circuit and determine the AC model parameters.
- Derive expressions for R_{in} , R_{out} , A_{voc} , A_v , A_i , G .
- Find R_{in} , R_{out} , A_{voc} , A_v , A_i , G .
- Find the output voltage waveform if $v_s = 10 \times 10^{-3} \sin(2\pi 5000t)$. Sketch the source and output voltage waveforms.
- Determine whether clipping will take place if $v_s = 25 \times 10^{-3} \sin(2\pi 5000t)$.

Q2

Consider the common-emitter BJT amplifier circuit shown in Figure 2.

Assume $V_{CC} = 15\text{ V}$, $\beta = 150$, $V_{BE} = 0.7\text{ V}$,

$R_E = 2.7\text{ k}\Omega$, $R_C = 4.7\text{ k}\Omega$, $R_1 = 47\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, $R_L = 47\text{ k}\Omega$, $R_s = 100\ \Omega$.

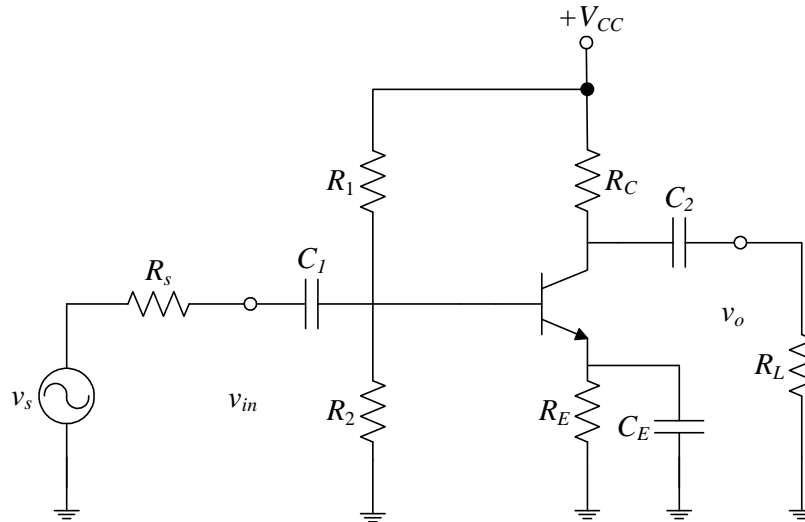


Figure 2: The circuit for Question 2.


- Determine the Q-point.
- Sketch the DC load-line. What is the maximum (peak to peak) output voltage swing available in this amplifier.
- Draw the AC equivalent circuit and determine the AC model parameters.
- Derive expressions for R_{in} , R_{out} , A_{voc} , A_v , A_i , G .
- Find R_{in} , R_{out} , A_{voc} , A_v , A_i , G .
- Find the output voltage waveform if $v_s = 10 \times 10^{-3} \sin(2\pi 5000t)$. Sketch the source and output voltage waveforms.

AUSTRALIAN NATIONAL UNIVERSITY
Department of Engineering

ENGN 2211 Electronic Circuits and Devices
Problem Set #8 Solution

Q1**Complete Solution**

Given that $V_{CC} = 15\text{ V}$, $\beta = 150$, $V_{BE} = 0.7\text{ V}$,
 $R_E = 1\text{ k}\Omega$, $R_C = 4.7\text{ k}\Omega$, $R_1 = 47\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, $R_L = 47\text{ k}\Omega$, $R_s = 100\ \Omega$.

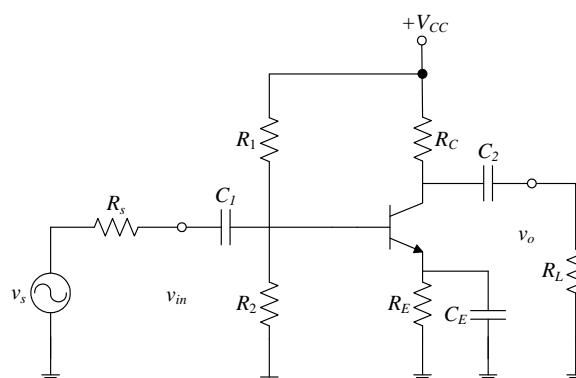**(a)**

Analyzing the DC Voltage-divider bias circuit, we have

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$= \frac{10\text{k}}{10\text{k} + 47\text{k}} (15) = 2.63\text{ V}$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

$$= \frac{(10\text{k})(47\text{k})}{10\text{k} + 47\text{k}} = 8.2456\text{ k}\Omega$$

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1)R_E}$$

$$= \frac{2.63 - 0.7}{8.2456\text{k} + (151)(1\text{k})} = 12.12\ \mu\text{A}$$

$$I_C = \beta I_B$$

$$= (150)(12.12\ \mu) = 1.8179\text{ mA}$$

$$I_E = (\beta + 1)I_B$$

$$= (151)(12.12\ \mu) = 1.83\text{ mA}$$

$$V_E = I_E R_E$$

$$= (1.83\text{m})(1\text{k}) = 1.83\text{ V}$$

$$V_C = V_{CC} - I_C R_C$$

$$= 15 - (1.8179\text{m})(4.7\text{k}) = 6.456\text{ V}$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$= 15 - (1.8179\text{m})(4.7\text{k}) - (1.83\text{m})(1\text{k}) = 4.626\text{ V}$$

As $I_B > 0$ and $V_{CE} > 0.2$ V, the transistor is in active region of operation.

The Q-point lies at

$$I_{CQ} = 1.8179 \text{ mA}$$

$$V_{CEQ} = 4.626 \text{ V}$$

(b)


For ideal cut-off

$$V_{CE(off)} = V_{CC} = 15 \text{ V}$$

For ideal saturation

$$I_{C(sat)} = \frac{V_{CC}}{R_C + R_E} = \frac{15}{5.7k} = 2.63 \text{ mA}$$

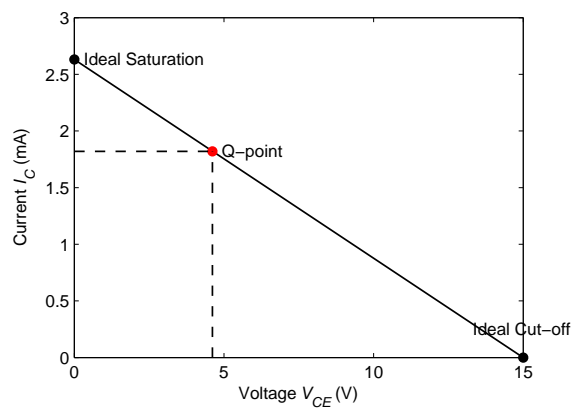
The plot of DC load line is shown in figure below




We see that the Q-point lies closer to saturation ($V_{CE} = 0.2$ V) than cut-off ($V_{CE} = 15$ V). Hence the maximum available peak to peak output voltage swing = $2(V_{CEQ} - 0.2) = 8.852$ V.

(c)

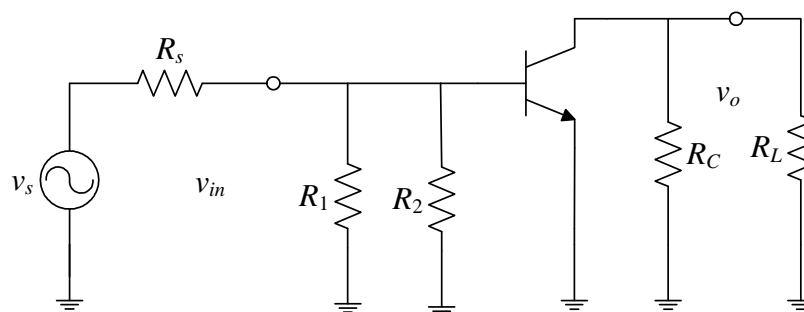Replacing the capacitors by short circuits and V_{CC} by virtual AC ground, the AC equivalent circuit is



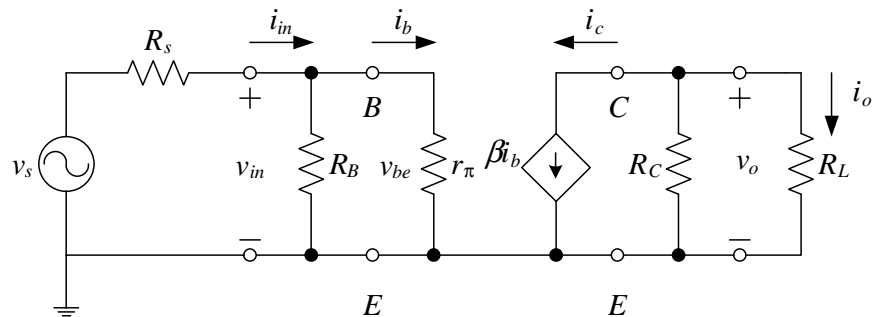Replacing the transistor by the small-signal AC equivalent circuit, we have



The AC Model parameters are

$$\begin{aligned}
 r_e &= \frac{26 \text{ mV}}{I_{EQ}} \\
 &= \frac{26}{1.83} = 14.207 \Omega \\
 r_\pi &= (\beta + 1)r_e \\
 &= (151)(14.207) = 2.1453 \text{ k}\Omega \\
 R_B &= R_1 || R_2 \\
 &= 8.2456 \text{ k}\Omega \\
 R'_L &= R_L || R_C \\
 &= (47 \text{ k}) || (4.7 \text{ k}) = 4.27 \text{ k}\Omega
 \end{aligned}$$

(d)

For derivations, please see Lecture 13.

(e)

The BJT CE amplifier parameters are

$$\begin{aligned}
 R_{in} &= R_B || r_\pi \\
 &= (8.2456 \text{ k}) || (2.1453 \text{ k}) = 1.7024 \text{ k}\Omega \\
 R_o &= R_C \\
 &= 4.7 \text{ k}\Omega \\
 A_{voc} &= -\frac{R_C \beta}{r_\pi} \\
 &= \frac{(4.7 \text{ k})(150)}{2.1453 \text{ k}} = -328.62 \\
 A_v &= -\frac{R'_L \beta}{r_\pi} \\
 &= \frac{(4.27 \text{ k})(150)}{2.1453 \text{ k}} = -298.56 \\
 A_i &= A_v \frac{R_{in}}{R_L} \\
 &= (-298.56) \frac{1.7024 \text{ k}}{47 \text{ k}} = -10.81 \\
 G &= A_i A_v \\
 &= (-10.81)(-298.56) = 3228.69
 \end{aligned}$$

(f)

Finding the equation for output voltage with load, we have

$$\begin{aligned}
 v_s &= 10 \times 10^{-3} \sin(2\pi 5000t) \\
 v_{in} &= \frac{R_{in}}{R_s + R_{in}} v_s \\
 &= \frac{1.7024 \text{ k}}{100 + 1.7024 \text{ k}} v_s \\
 &= 0.9445 v_s \\
 v_o &= A_v v_{in} \\
 &= (-298.56)(0.9445 v_s) \\
 &= (-298.56)(0.9445)(10 \times 10^{-3} \sin(2\pi 5000t)) \\
 &= -2.82 \sin(2\pi 5000t)
 \end{aligned}$$

The required peak to peak output voltage swing = $2(2.82) = 5.64 \text{ V}$.

The maximum available peak to peak output voltage swing = $8.852 \text{ V} > 5.64 \text{ V}$.

Hence no clipping will take place.

The -ve sign indicates that output voltage is 180° out of phase with input voltage (inverting amplifier).

The time period is $T = \frac{1}{5000} = 0.2 \text{ ms}$.

The sketch of input and output voltages is shown in figures below:- (Note y-axis has different units in the two figures)

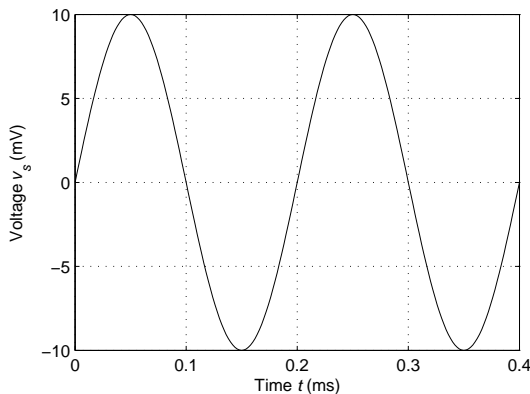


Figure 3: Source voltage $v_s(t)$.

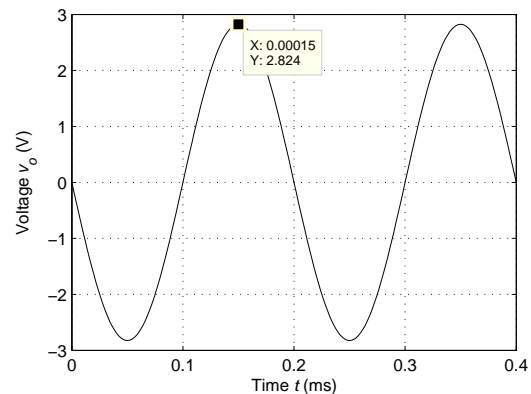


Figure 4: Output voltage $v_o(t)$.

(g)

For $v_s = 25 \times 10^{-3} \sin(2\pi 5000t)$, we have

$$\begin{aligned}
 v_o &= A_v v_{in} \\
 &= (-298.56)(0.9445 v_s) \\
 &= (-298.56)(0.9445)(25 \times 10^{-3} \sin(2\pi 5000t)) \\
 &= -7.05 \sin(2\pi 5000t)
 \end{aligned}$$

The required peak to peak output voltage swing = $2(7.05) = 14.1 \text{ V}$.


However the maximum available peak to peak output voltage swing = $8.852 \text{ V} < 14.1 \text{ V}$.

Hence clipping will take place.

See ProbSet08_Q1 . sch.

Q2**Solution**

Given that $V_{CC} = 15\text{ V}$, $\beta = 150$, $V_{BE} = 0.7\text{ V}$,
 $R_E = 2.7\text{ k}\Omega$, $R_C = 4.7\text{ k}\Omega$, $R_1 = 47\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, $R_L = 47\text{ k}\Omega$, $R_s = 100\text{ }\Omega$.

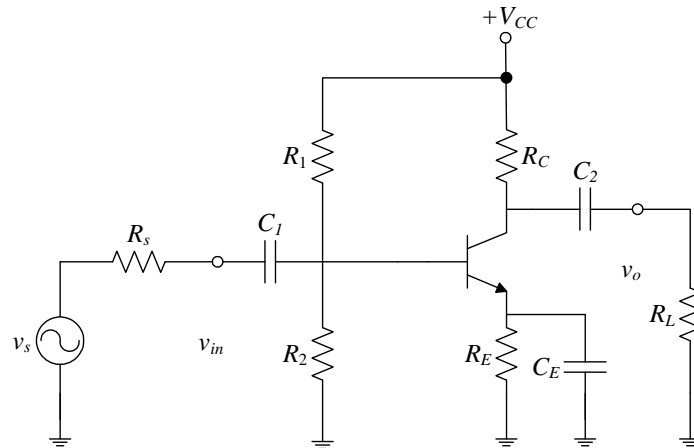**(a)**

Analyzing the DC Voltage-divider bias circuit, we have

$$\begin{aligned} V_{TH} &= 2.63\text{ V} \\ R_{TH} &= 8.2456\text{ k}\Omega \\ I_B &= 4.64\text{ }\mu\text{A} \\ I_C &= 0.696\text{ mA} \\ I_E &= 0.7006\text{ mA} \\ V_C &= 11.72\text{ V} \\ V_E &= 1.89\text{ V} \\ V_{CE} &= 9.837\text{ V} \end{aligned}$$

As $I_B > 0$ and $V_{CE} > 0.2\text{ V}$, the transistor is in active region of operation.

The Q-point lies at

$$\begin{aligned} I_{CQ} &= 0.696\text{ mA} \\ V_{CEQ} &= 9.837\text{ V} \end{aligned}$$


(b)

For ideal saturation and cut-off

$$V_{CE(off)} = 15 \text{ V}$$

$$I_{C(sat)} = 2.027 \text{ mA}$$

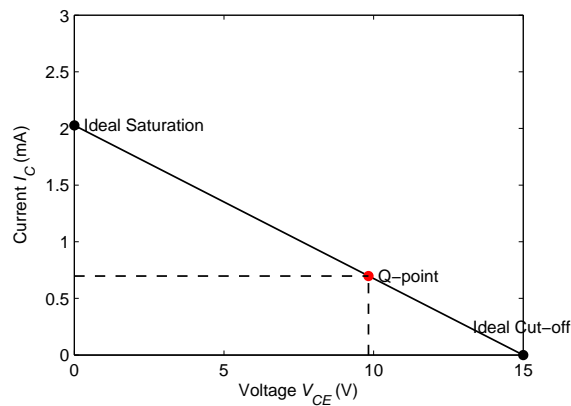The plot of DC load line is shown in figure below



We see that the Q-point lies closer to cut-off ($V_{CE} = 15 \text{ V}$) than saturation ($V_{CE} = 0.2 \text{ V}$). Hence the maximum available peak to peak output voltage swing $= 2(V_{CC} - V_{CEQ}) = 10.34 \text{ V}$.

(c)

The AC Model parameters are

$$r_e = 37.11 \ \Omega$$

$$r_\pi = 5.6037 \text{ k}\Omega$$

$$R_B = 8.2456 \text{ k}\Omega$$

$$R'_L = 4.27 \text{ k}\Omega$$

(d)

For derivations, please see Lecture 13.

(e)

The BJT CE amplifier parameters are

$$R_{in} = 3.336 \text{ k}\Omega$$

$$R_o = 4.7 \text{ k}\Omega$$

$$A_{voc} = -125.81$$

$$A_v = -114.3$$

$$A_i = -8.11$$

$$G = 926.97$$

(f)

$$v_s = 10 \times 10^{-3} \sin(2\pi 5000t)$$

$$v_{in} = 0.97089v_s$$

$$v_o = -1.11 \sin(2\pi 5000t)$$

The required peak to peak output voltage swing = $2(1.11)=2.2$ V.

The maximum available peak to peak output voltage swing = 10.34 V $>$ 2.2 V.

Hence no clipping will take place.

The sketch of input and output voltages is shown in figures below:- (Note y-axis has different units in the two figures)

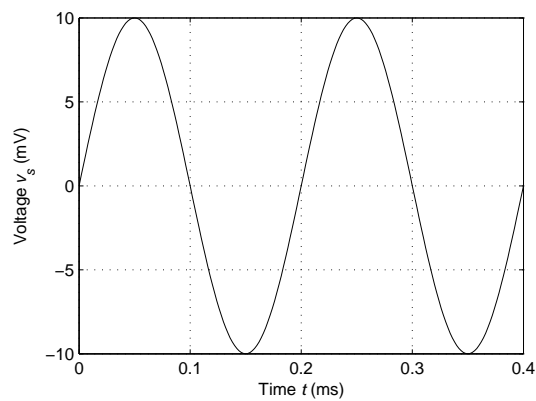


Figure 5: Source voltage $v_s(t)$.

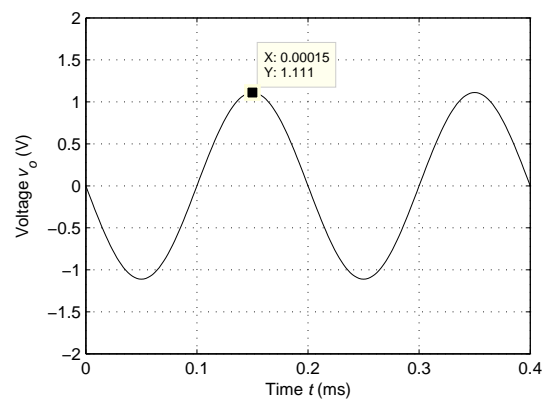


Figure 6: Output voltage $v_o(t)$.

See ProbSet08_Q2 . sch.