## **Transistors at Radio Frequency**

- ► How to describe transistors at radiofrequency.
- Equivalent circuits and S-parameters
- Y-parameters and SOLVE
- Stability of transistor amplifiers (brief)
- ► The Klapp RF Oscillator
- SOLVE Example: The Klapp Oscillator



## **Transistors at Radio Frequency**

- Transistors are more complex at high frequencies due to the effects of internal parasitic inductance and capacitance.
- Always try first to seek S-parameters from manufacturers.
- Or use a simulation package that has them in its database.
- ► Failing all this.. do a model. Here's how.
- We try to glean enough information from datasheets and independent measurements to form a physical model to predict S-parameters.



### **BF199 VHF Transistor**

Philips Semiconductors

#### NPN medium frequency transistor

#### FEATURES

- · Low current (max. 25 mA)
- · Low voltage (max. 25 V).

#### APPLICATIONS

· Output stage of a vision IF amplifier.

#### DESCRIPTION

NPN medium frequency transistor in a TO-92; SOT54 plastic package.

#### PINNING

PIN	DESCRIPTION	
1	base	
2	emitter	
3	collector	

Product specification

BF199



#### QUICK REFERENCE DATA

SYMBOL	PARAMETER	CONDITIONS	MIN.	TYP.	MAX.	UNIT
V <sub>CBO</sub>	collector-base voltage	open emitter	-	-	40	٧
V <sub>CEO</sub>	collector-emitter voltage	open base	-	-	25	V
I <sub>CM</sub>	peak collector current		-	-	25	mA
Ptot	total power dissipation	$T_{amb} \le 25 ^{\circ}C$	-	-	500	mW
h <sub>FE</sub>	DC current gain	$I_C = 7 \text{ mA}; V_{CE} = 10 \text{ V}$	38	-	-	
f <sub>T</sub>	transition frequency	$I_C = 5 \text{ mA}; V_{CE} = 10 \text{ V}; f = 100 \text{ MHz}$	-	550	-	MHz



# **Radio Frequency Transistor circuit model**





### **BF199 Datasheet**

Product specification

#### NPN medium frequency transistor

BF199

#### LIMITING VALUES

Philips Semiconductors

In accordance with the Absolute Maximum Rating System (IEC 134).

SYMBOL	PARAMETER	CONDITIONS	MIN.	MAX.	UNIT
V <sub>CBO</sub>	collector-base voltage	open emitter	-	40	v
VCEO	collector-emitter voltage	open base	-	25	v
VEBO	emitter-base voltage	open collector	-	4	v
lc .	collector current (DC)		-	25	mA
I <sub>CM</sub>	peak collector current		-	25	mA
Ptot	total power dissipation	T <sub>amb</sub> ≤ 25 °C; note 1	-	500	mW
Tstg	storage temperature		-65	+150	°C
Тį	junction temperature		-	150	°C
T <sub>amb</sub>	operating ambient temperature		-65	+150	°C

#### Note

1. Transistor mounted on an FR4 printed-circuit board.

#### THERMAL CHARACTERISTICS

	SYMBOL	PARAMETER	CONDITIONS	VALUE	UNIT
1	R <sub>h j-a</sub>	thermal resistance from junction to ambient	note 1	250	ĸw

Note

1. Transistor mounted on an FR4 printed-circuit board.

#### CHARACTERISTICS

Tarrb = 25 °C unless otherwise specified.

SYMBOL	PARAMETER	CONDITIONS	MIN.	TYP.	MAX.	UNIT
lcao	collector cut-off current	IE = 0; VCB = 40 V	-	-	100	nA
leao	emitter cut-off current	I <sub>C</sub> = 0; V <sub>EB</sub> = 4 V	-	-	100	nA
h <sub>FE</sub>	DC current gain	I <sub>C</sub> = 7 mA; V <sub>CE</sub> = 10 V	38	-	-	
VBE	base-emitter voltage	I <sub>C</sub> = 7 mA; V <sub>CE</sub> = 10 V	-	775	925	mV
Cre	feedback capacitance	I <sub>C</sub> = 0; V <sub>CB</sub> = 10 V; f = 1 MHz	-	-	0.5	рF
fT	transition frequency	I <sub>C</sub> = 5 mA; V <sub>CE</sub> = 10 V; f = 100 MHz	-	550	-	MHz





### **Networks: Y-parameters vs S-parameters**

> Y-parameters and S-parameters are related:  $y_i = \frac{(1+S_{22})(1-S_{11}) + S_{12}S_{21}}{\Lambda Z_0}$  $y_r = \frac{-2S_{12}}{\Lambda Z_0}$  $y_f = \frac{-2S_{21}}{\Lambda Z_0}$  $y_o = \frac{(1+S_{11})(1-S_{22}) + S_{12}S_{21}}{\Delta Z_0}$ where  $\Delta = (1 + S_{11})(1 + S_{22}) - S_{21}S_{12}$ .



# **Definition of Y-parameters**

Need these for employ solve.

$$I_i = y_i V_{eb} + y_r V_{ec}$$

$$I_o = y_f V_{eb} + y_o V_{ec}$$





# **Using Solve For Transistors**

















# **Example: A BF199 Common Emitter Amplifier**

- Use the large signal equivalent (left) to set the bias point.
- Use the small signal equivalent (right) to set up SOLVE.





# **Stability Criteria**

Is the transistor stable in isolation? Linville criterion

$$C = \frac{|y_r y_f|}{2g_i g_r - real(y_r y_f)}$$

Often we need to know if a transistor amplifier is stable.

► If a transistor with given y-parameters is loaded by source and load admittances  $Y_S = G_S + jB_S$  and  $Y_L = G_L + jB_L$ , then the transistor circuit is unconditionally stable if,

$$K = \frac{2(g_i + G_S)(g_o + G_L)}{|y_r y_f| + real(y_r y_f)} > 1$$

# The Stern Stability Criterion

A number of useful related formulae.. see the web brick.



# **Klapp RF Oscillator**

- Model the transistor using S and Y parameters in exactly the same way as the transistor amplifier.
- In the project the oscillator is a VCO: the MC145170 PLL has to control the frequency of the oscillator by applying a voltage to a varactor diode or voltage variable capacitor (VVC).
- > We need to prove that the oscillator will oscillator and at what frequency.
- In SOLVE we inject a current into the tank circuit of the oscillator and determine the frequency at which the ractance of the input impedance is zero and the resisitance is negative. WHY?



# **Varactor Diode**



Diode capacitance  $C_T = f(V_R)$ f = 1 MHz



# Klapp RF Oscillator





### **Using SOLVE: Compute S-parameters and Y-parameters**

```
% The parameters of the oscillator circuit
%Step 1 Run S_parameters to generate the S-parameters for
% the transistor.
clear all
S_parameters_BF199
det = (1 + S11) \cdot (1 + S22) - S21 \cdot S12;
%Step 2 calculate the y-parameters
yi = ((1 + S22) \cdot (1 - S11) + S12 \cdot S21) \cdot /det/Z0;
yr = -2*S12./det/Z0;
vf = -2*S21./det/Z0;
y_0 = ((1 + S_{11}) \cdot (1 - S_{22}) + S_{12} \cdot S_{21}) \cdot (det/Z_0);
                   %number of nodes
N = 6;
y = zeros(N,N,Nvals); %The admittances
omega = 2*pi*frequency;
```



**Using SOLVE: Set circuit values** 

```
CT = 2e - 12;
LT = 8000.e-9;
CLT = .1e - 12;
\overline{Z}CLT = 1./j./omega/CLT;
ZLT = 1.+j*omega*LT;
ZT = (ZCLT.*ZLT)./(ZCLT + ZLT) + 1./j./omega/CT;
YT = 1./ZT;
C1 = 10.0e - 12;
Z1 = 1/j./omega/C1;
C2 = 20.0e - 12;
Z2 = 1/j./omega/C2;
R1 = 43.;
R2 = 3300.;
RL = 50.;
```



### **Using SOLVE: Set SOLVE admittances**

```
y(1,2,:) = YT;
y(2,1,:) = YT;
y(3,2,:) = 1./Z1;
y(2,3,:) = 1./Z1;
y(4,2,:) = yi+yr;
y(5,2,:) = -yr;
y(2,3,:) = 1./Z1;
y(3,2,:) = 1./Z1;
y(4,3,:) = 1/R1;
y(3,4,:) = 1/R1;
y(6,3,:) = 1/R2 + 1./Z2;
y(3,6,:) = 1/R2 + 1./Z2;
y(2,4,:) = yi+yf;
y(5,4,:) = yr+yo;
y(3,4,:) = 1/R1;
y(4,3,:) = 1/R1;
y(2,5,:) = -yf;
y(4,5,:) = yf+yo;
y(6,5,:) = 1/RL;
y(5,6,:) = 1/RL;
```



# **KLAPP oscillator input impedance**



