More on Four Ports

- Theorems of four port networks
- ▶ 180 ° and 90° Hybrids
- Directional couplers
- > Transmission line transformers, Four port striplines
- > 90° phase shifters.
- Baluns
- Wilkinsons, Magic-T's



Fundamentals of Four Port Devices

Consider the four port network with scattering matrix...

$$\begin{pmatrix} a_2 \\ b_2 \\ c_2 \\ d_2 \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} & S_{13} & S_{14} \\ S_{21} & S_{22} & S_{23} & S_{24} \\ S_{31} & S_{32} & S_{33} & S_{34} \\ S_{41} & S_{42} & S_{43} & S_{44} \end{pmatrix} \begin{pmatrix} a_1 \\ b_1 \\ c_1 \\ d_1 \end{pmatrix}$$





Power Dividers and Combiners

- > Assume the four port is matched then $S_{11} = 0, S_{22} = 0, S_{33} = 0$ and $S_{44} = 0$
- Solution Assume that from any port, half the power appears at two other ports. For example consider waves propagating from ports A and B to ports C and D with phase shifts ϕ_{AC} , ϕ_{AD} , ϕ_{BC} and ϕ_{BD} .

$$V_C = \frac{1}{\sqrt{2}} \exp j\phi_{AC} + \frac{1}{\sqrt{2}} \exp j\phi_{BC}$$

$$V_D = \frac{1}{\sqrt{2}} \exp j\phi_{AD} + \frac{1}{\sqrt{2}} \exp j\phi_{BD}$$

Power conservation implies that

$$2 = 2 + \cos \left(\phi_{AC} - \phi_{BC}\right) + \cos \left(\phi_{AD} - \phi_{BD}\right)$$

or $\cos \left(\phi_{AC} - \phi_{BC}\right) + \cos \left(\phi_{AD} - \phi_{BD}\right) = 0$



The 180° and 90° Hybrids

> We distinguish two cases, ($\phi_{AC} = 0^{o}$, $\phi_{AD} = 0^{o}$) and ($\phi_{AC} = 0^{o}$, $\phi_{AD} = 90^{o}$).





The 90° Hybrids



Figure 6. Microwave Frequency 90° Hybrid Schematics and Phase Truth Table



Transmission Line Transformers

- ► One way to make 180^o Hybrids.
- > Transformers and transmission lines are equivalent at Radiofrequency!





Rules for Transmission Line Transformers

> Always wind the windings in multifilar fashion.

- Can use either toroidal or linear or whatever shaped ferrites. Toroidal ferrites are usually the best.
- The dot on the transformer diagram points to one end of the wires at one end of the transformer.
- ► The voltage drop across all windings must be same. WHY?
- The currents in the same direction in the windings must sum to zero.
 WHY?

Respects phase delays along the transmission line when doing its sums?



Transmission Line Transformer 180⁰ Hybrid





The Linear Phase Shift Combiner.





The Magic-T (Wilkinson)

The magic-T is a three port device that uses lossiness in order to achieve reciprocity and matching.





The Magic-T (Wilkinson)





Wilkinson Combiner





Lumped Component Wilkinson Splitter/Combiner





A 90^o Phase Shifter

- Basic building block as shown.
- Need to use two of these in parallel arms to get a *relative* phase shift of a fixed amount over a wide range of frequencies.
- > Ideal for connecting to a 180° hybrid in order to make a 90° hybrid.





A 90^o Phase Shifter

To design let ω_p designate the operating frequency, $C = 2/(\omega_p Z_o)$ and $L = Z_o/(2\omega_p)$, then it can be shown that the transfer function of one stage is given by,

$$\frac{V_o}{V_i} = \frac{1 + \omega^2 LC}{1 - \omega^2 LC + 4j\omega L/Z_o} = \frac{1 - j\omega/\omega_p}{1 + j\omega/\omega_p}$$

- > Usually use two of these driven in parallel so that the output phases track each other. Need to stagger ω_p values.
- > Input impedance exactly Z_o if terminated in Z_o .
- If V₁ and V₂ are in phase then the outputs are 90° out of phase (in quadrature). Note that the phase of each output with repect to either input is quite variable.





A 90^o Phase Shifter

> ω_p = 4.4383e+08 and 7.0529e+07 rads/sec





A 90^o Phase Hybrid Implementation





A Simple Directional Coupler

▶ Travelling waves on the line obey V_f = Z_oI_f and V_r = -Z_oI_r
 ▶ Thus a linear combination of the total voltage V and I can be used to separately obtain V_f and V_r.





BALUNS

- ► Used to transform impedance and balance.
- Respects phase: Guanella G. 'Novel Matching Systems for High Fequencies,' Brown-Boverie Review, Vol 31, September 1944, Pages 327-329
- Does not respect phase: Ruthroff CL, 'Some Broad-Band Transformers', Proc IRE, Vol 47, August 1959, pages 1337-1342
- BALUNS Use to match unbalanced to balanced lines (vice versa).
- UNUNS Use to match unbalanced to unbalanced lines.



Balanced and Unbalanced Systems

- A Balanced system is one which is symmetric or push-pull with respect to voltage drive. An Unbalanced system usually means one which is connected to earth and therefore cannot be driven.
- How do we connect the balanced antenna or trasnmission line to the unbalanced coaxial transmission line?
- Need to respect the differential voltage drive required by balanced loads when driving from an unbalanced source.











Ruthroff Baluns

- Do not repect phase delays.
- > 1:4 Impedance matching unun (left) and balun (right).





Guanella Baluns

- > Do repect phase delays.
- > 1:4 Impedance matching balan.





EXAMPLE WELL KNOWN BALUN

• Use the following to connect your unbalanced 300 Ω antenna or cable to a balanced 75 Ω cable or TV set.



