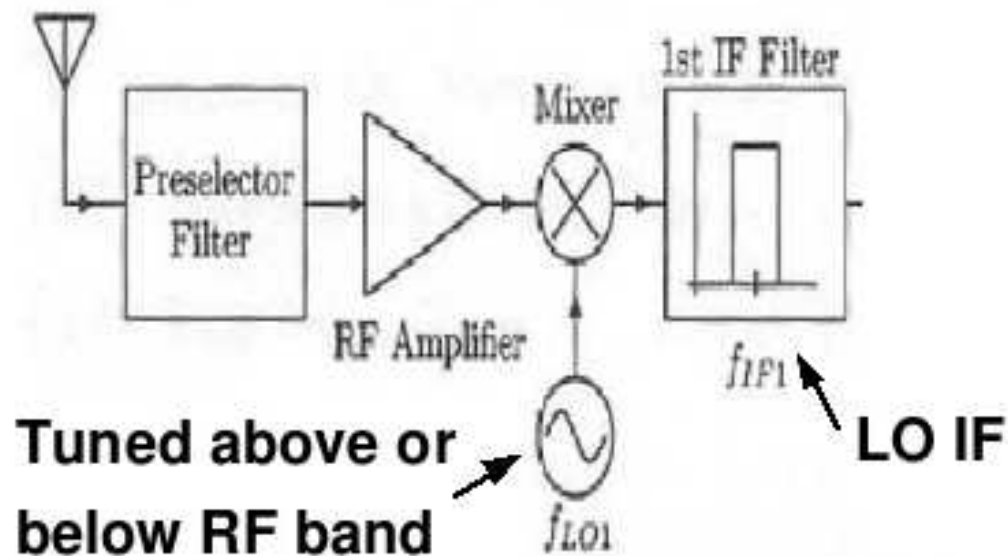


Project ENGN4545


- Project description
- Introduction to the Radiofrequency chips used in the projects.
- Review of Lecture10

Low Intermediate Frequency Receiver

- The LOW IF can be digitised to avoid the 90° phase shifter.
- Has an image problem like all superhets.



Transceiver 1

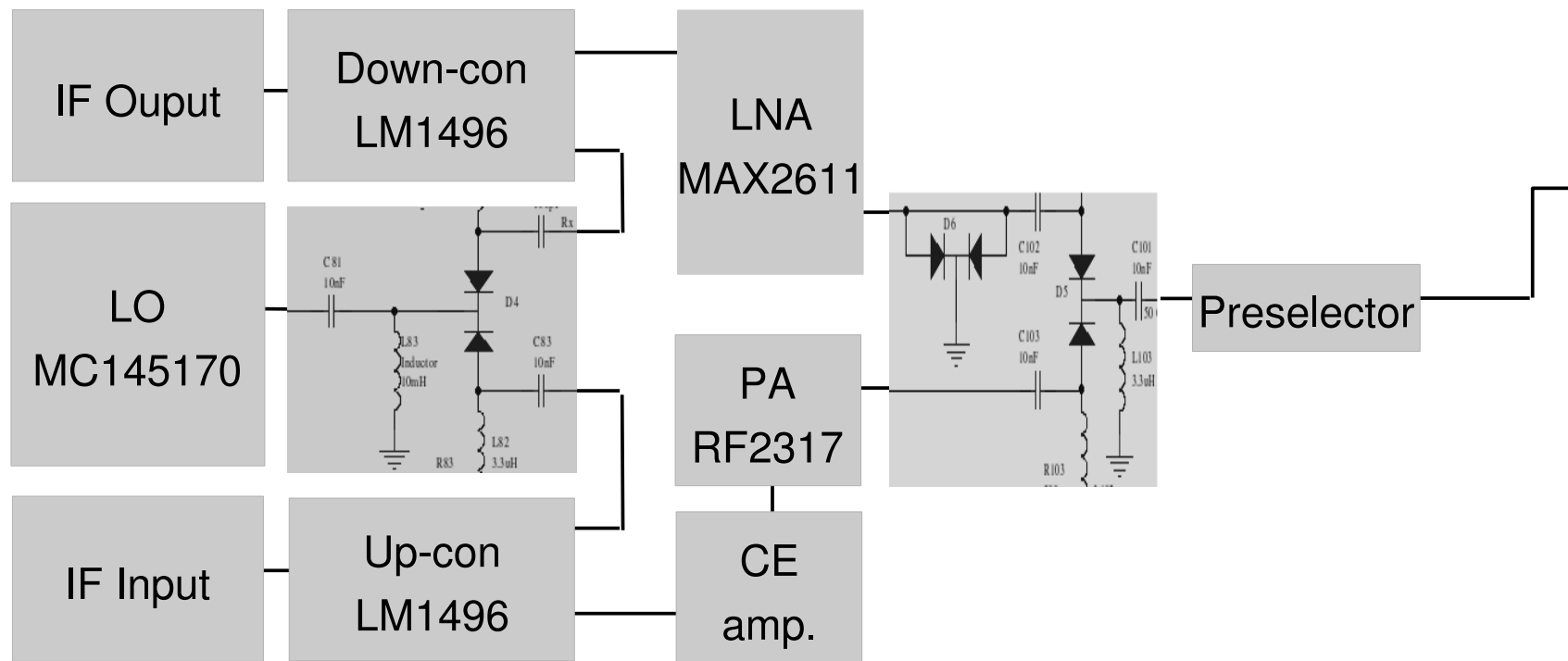


Transceiver 1

- Worth 40% of mark.
- Mark of 60% of this for the logbook, scrap book and description and dead bug results for the frequency synthesiser.
- 20% for the PCB layout design and description (Eagle files).
- 20% for the working circuit and tests.
- Need eagle PCB designs in by the end of the week.


Mixers

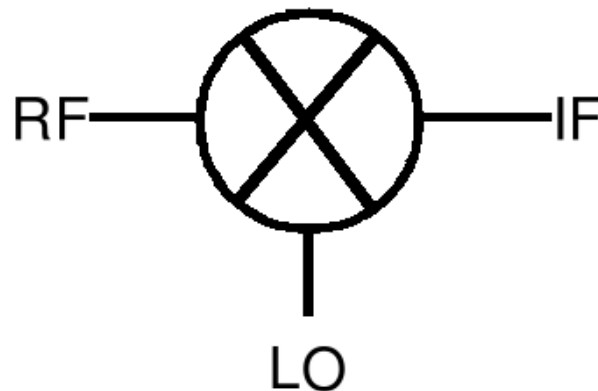- Mathematically, mixers are multipliers.
- Terminology in the following figure and loosely: $IF = RF \times LO$.
- Multiplication of sine waves produces sines waves of different frequencies (trig formulae).



LM1496 Balanced Modulator Demodulator

- VHF frequencies only.

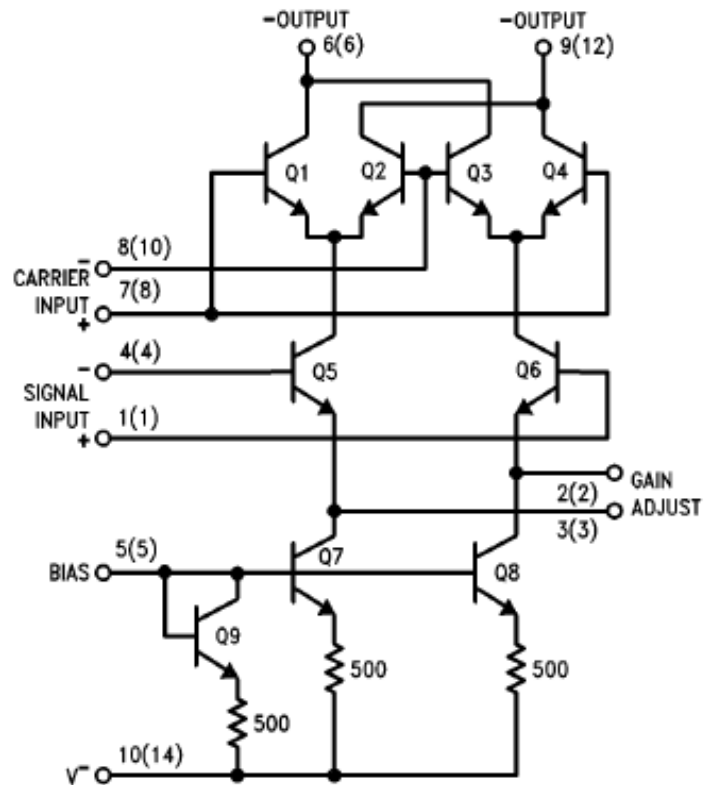

Numbers in parentheses show DIP connections.

LM1496 Balanced Modulator Demodulator: How does it work



MAX2611 LNA

19-1094; Rev 2; 4/05

EVALUATION KIT
AVAILABLE

MAXIM

DC-to-Microwave, Low-Noise Amplifier

General Description

The MAX2611 is a low-voltage, low-noise amplifier for use from DC to microwave frequencies. Operating from a single +5V supply, it has a 3dB bandwidth of 1100MHz. The MAX2611's low noise figure and high drive capability make it ideal for a variety of transmit, receive, and buffer applications.

In a typical application, the only external components needed are input and output blocking capacitors and a VCC series resistor. To improve gain and output power, an RF choke can be added in series to the bias resistor.

The MAX2611 comes in a 4-pin SOT143 package, requiring minimal board space.


Features

- ◆ Single +5V Supply Operation
- ◆ 3dB Bandwidth: DC to 1100MHz
- ◆ High Gain: 18dB at 500MHz
- ◆ Low Noise Figure: 3.5dB at 500MHz
- ◆ High Drive Capability: +3dBm at 16mA I_D
- ◆ Ultra-Small SOT143 Package


MAX2611

MAX2611 LNA

Typical Operating Circuit

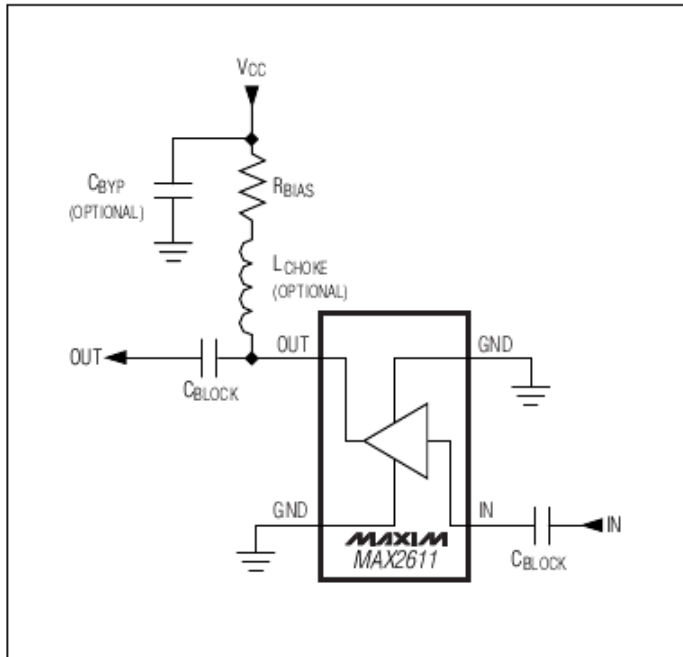


Pin Configuration

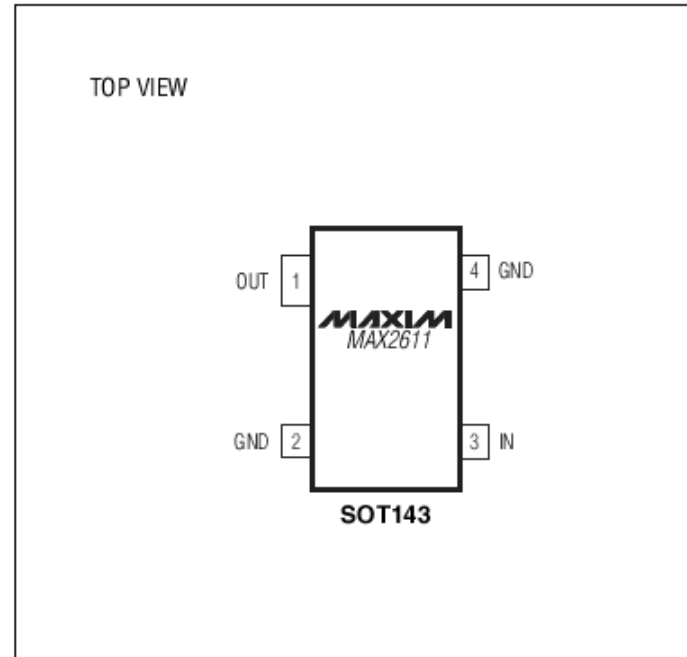

RF2317

Evaluation Board Schematic - 50 Ω

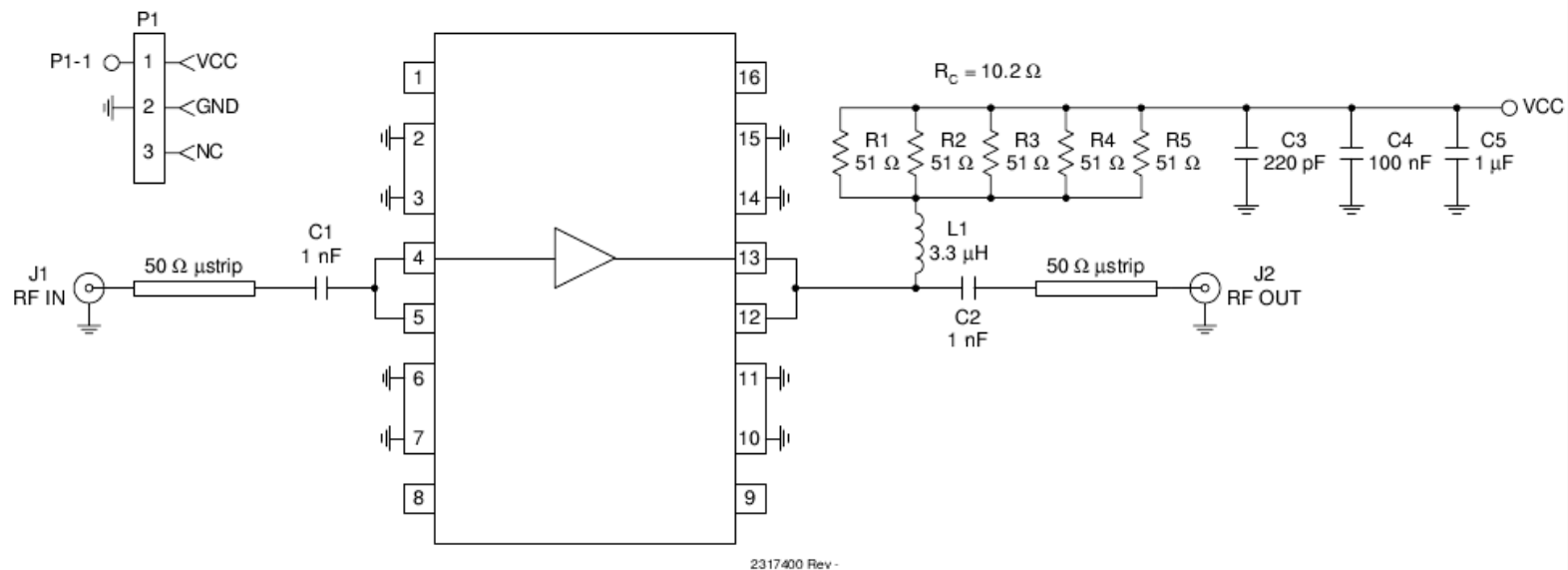(Download [Bill of Materials](http://www.rfmd.com) from www.rfmd.com.)



PIN diodes


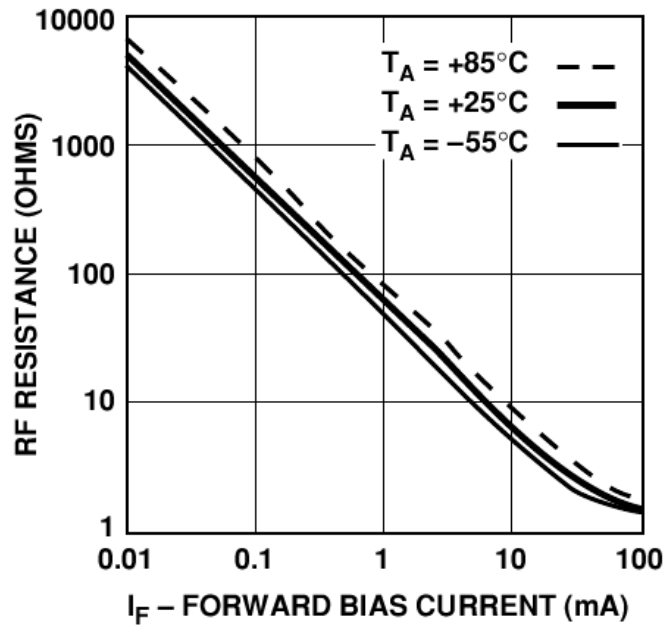
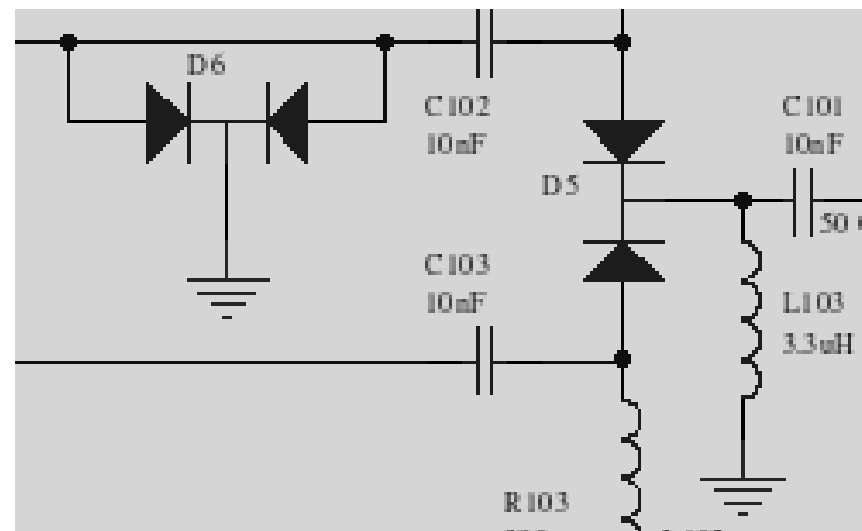


Figure 2. RF Resistance vs. Forward Bias Current.

PIN diodes

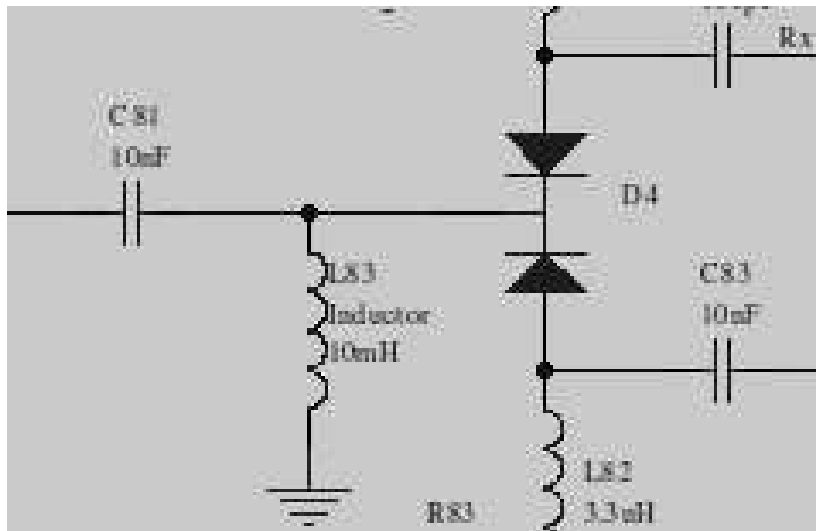


Frequency Synthesisers

- Phase lock loop (PLL) and voltage controlled oscillator (VCO)
- Direct Digital Synthesiser (DDS).


The MC145170

- Operates up to 185 MHz. But no internal VCO.
- R Counter Division Range: 1 and 5 to 32,767
- N Counter Division Range: 40 to 65,535
- Special patented bit grabbing interface to set the PLL parameters such as N and R prescaler values.


The MC145170

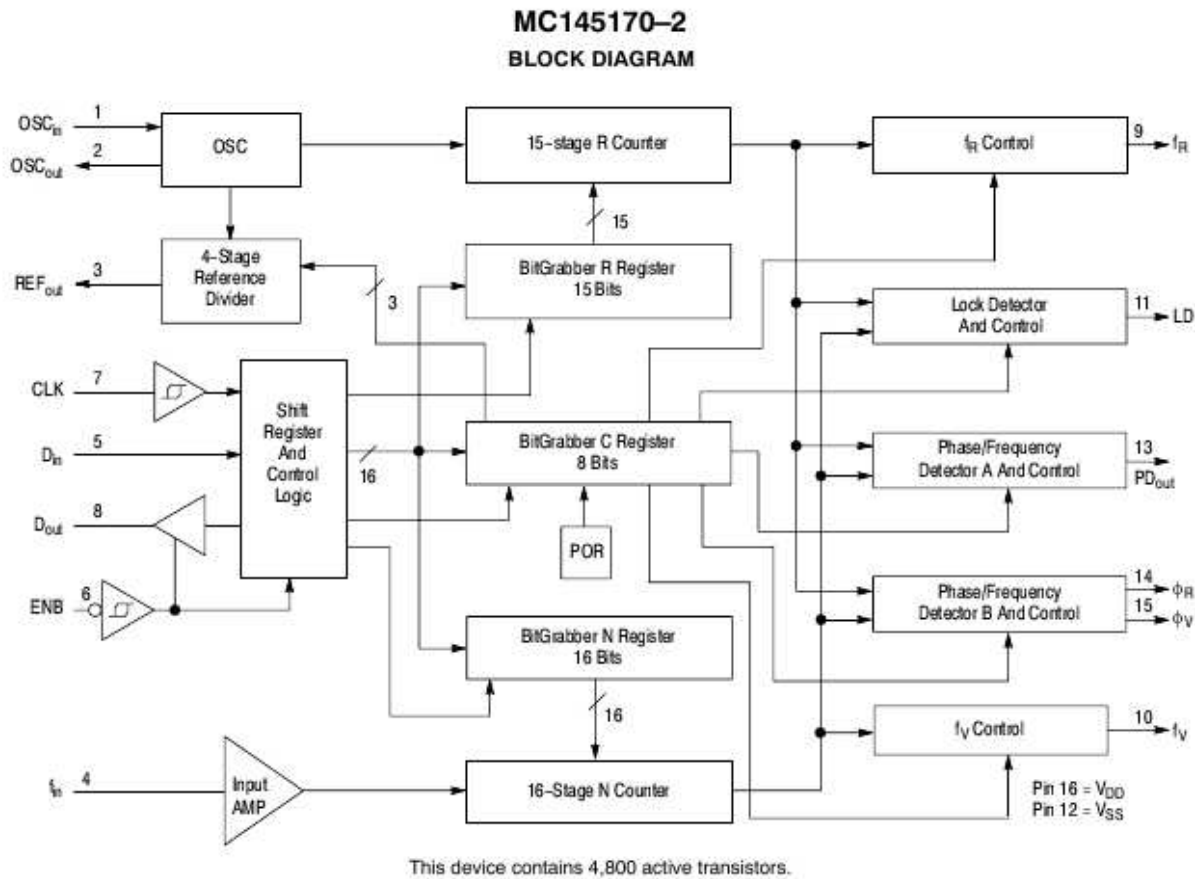


The Voltage Controlled Oscillator

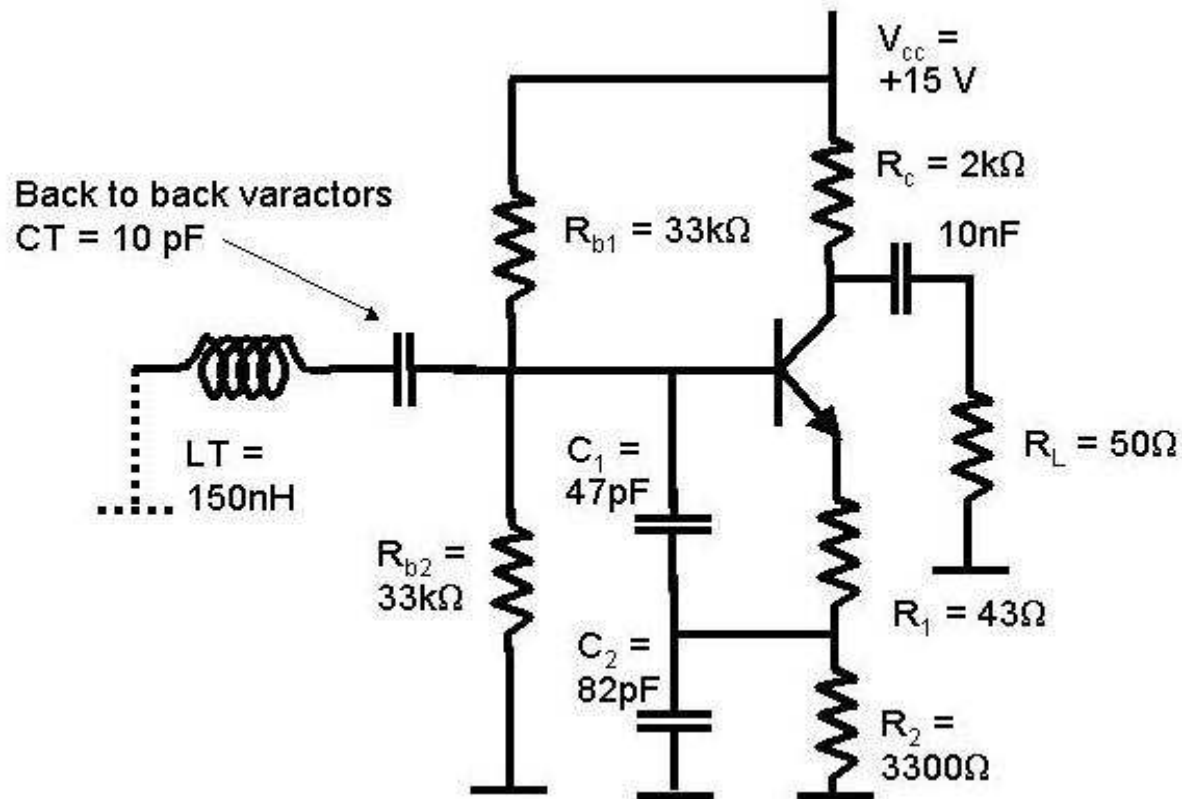

The Modulator

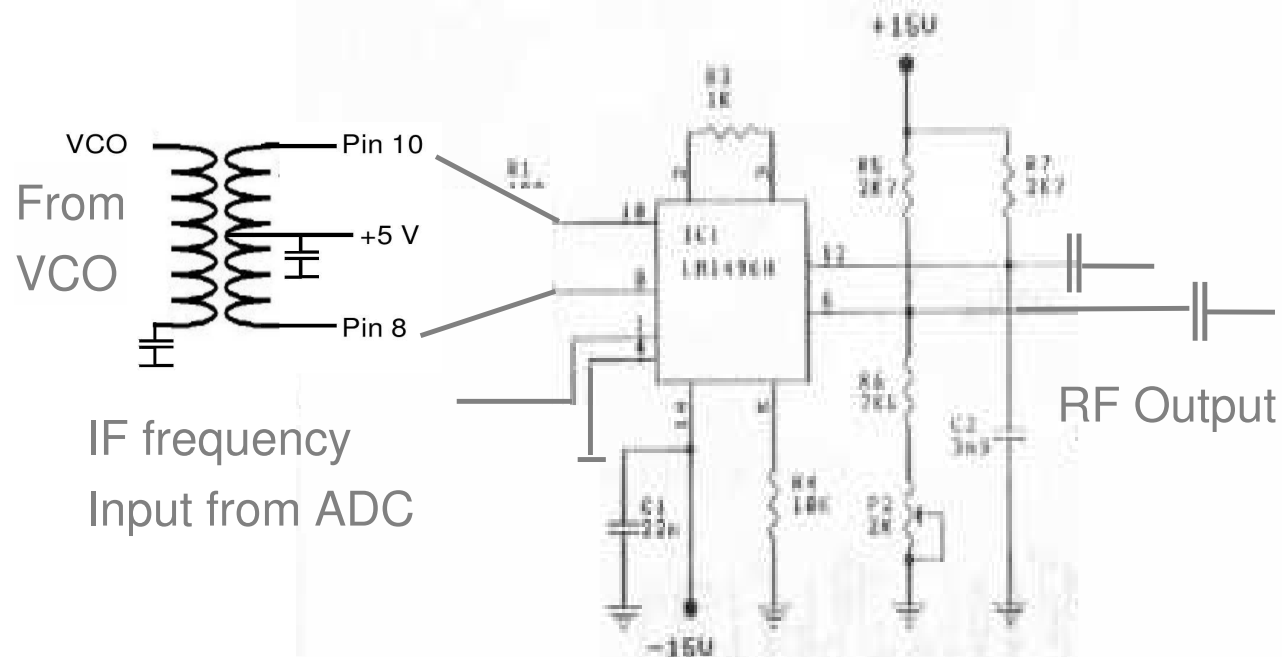

Transceiver 2

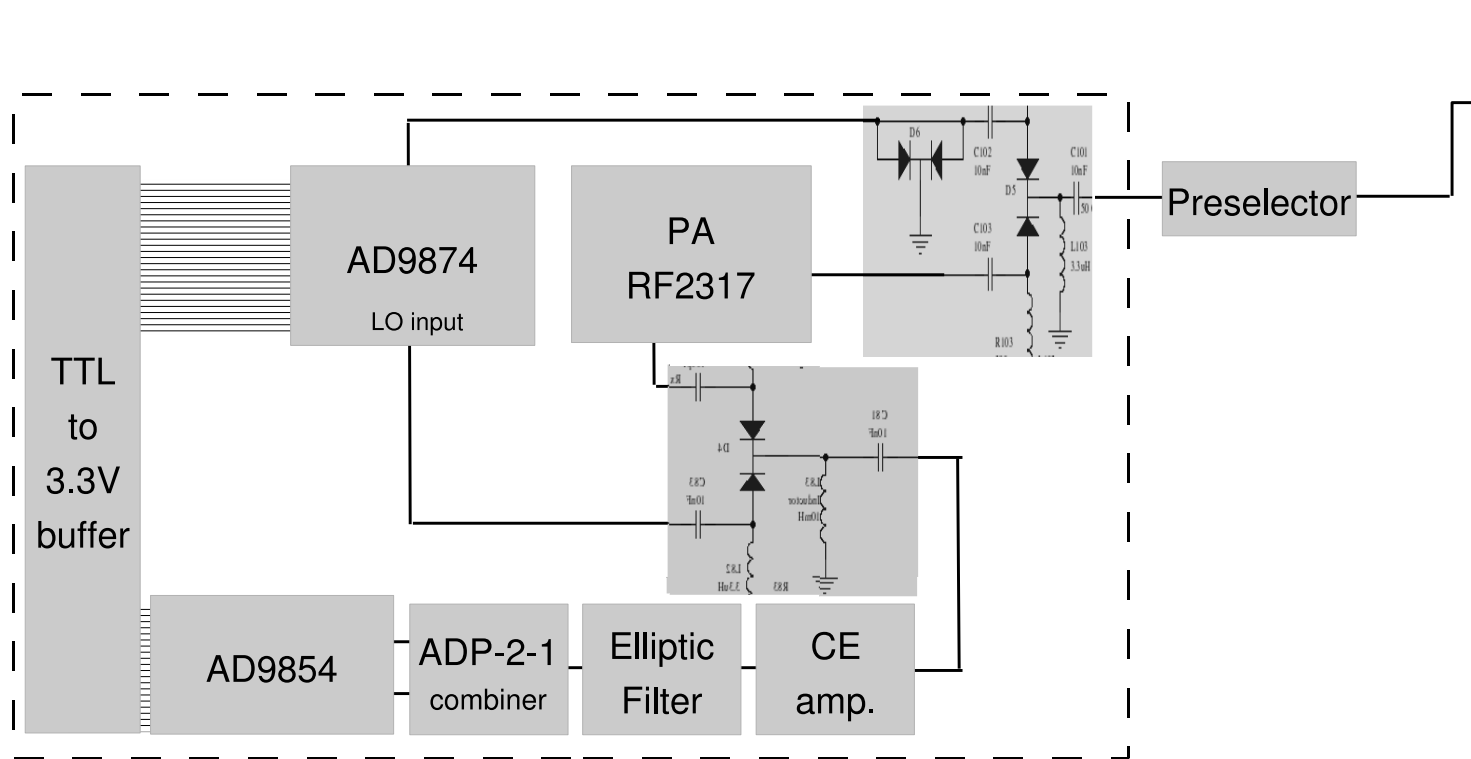


Transceiver 2


- Integrated. Plug-n-play.
- Need to read the datasheets for the AD9854 and AD9874 carefully.
- Also read <http://www.arrl.org/tis/info/pdf/030304qex020.pdf>
- Cheaper and faster in the long run.
- Ideal for those who wish to experience state of the art and are good at RF PCB design and soldering.
- Cannot do a breadboard dead-bug prototype. Start with a PCB layout. I.E. start EAGLE (or whatever) design immediately.

Transceiver 1


- Worth 40% of mark.
- 40% For logbook and scrapbook and general description in the report.
- 40% for the PCB layout design and description (Eagle files).
- 20% for the working circuit and tests.
- Need eagle PCB designs in by the end of the week.

AD9854 Direct Digital Synthesiser

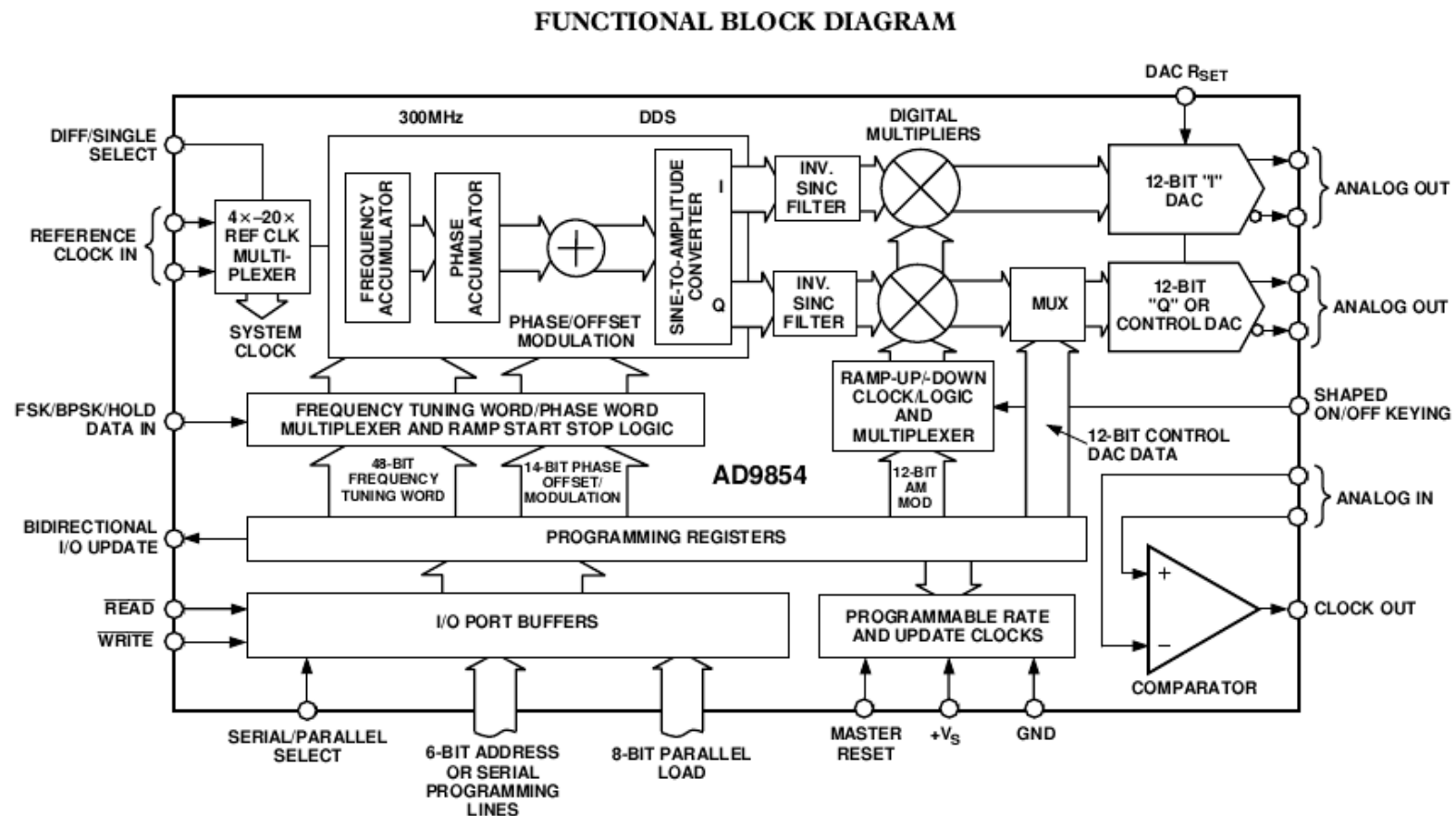

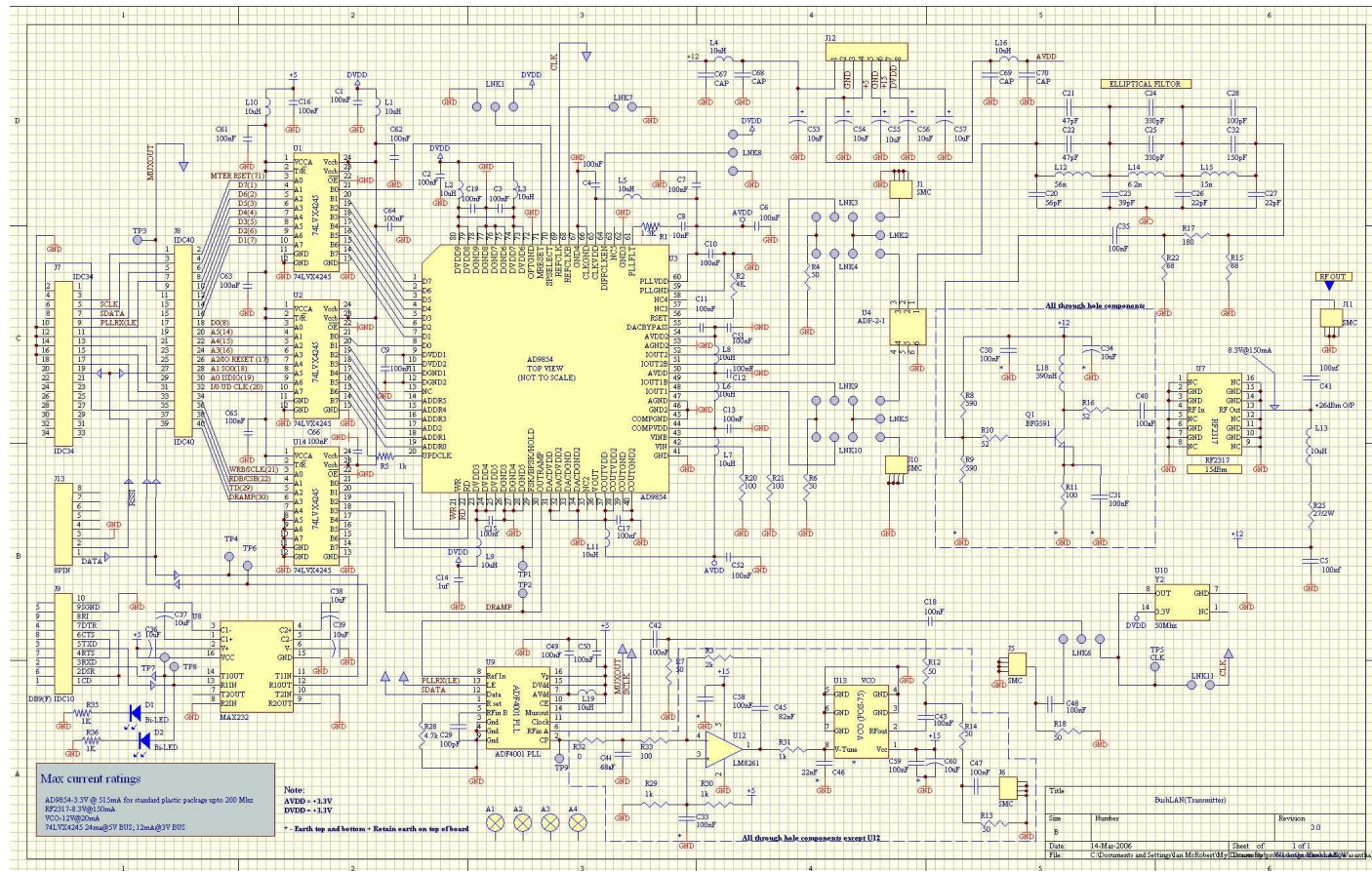

AD9854 Layout

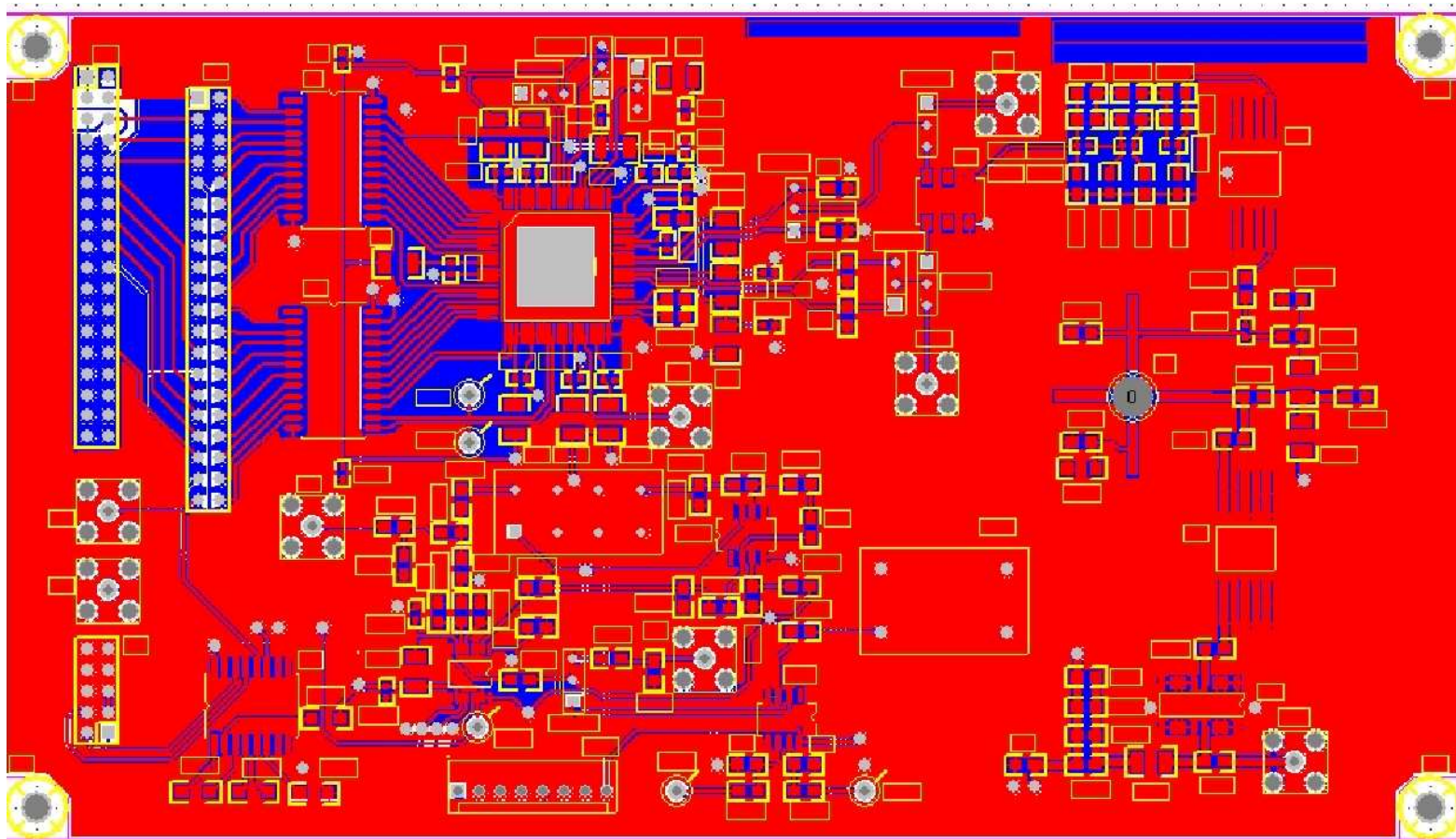

AD9874 IF Digitising Subsystem



- Input impedance about $400\ \Omega$. See p 22 of the data sheet.
- DOUTA/DOUTB are differential outputs. Suggest AD8561 capacitor as on the Eval Board schematic.
- Very important to have a ground plane on the lower layer.
- Don't forget about decoupling caps for power supply
- Separate the AVDD and DVDD.
- Lots of IO = 37 in total.
- Do we need to have IO buffering? If not we need to provide DVDD on the IDC connector pin.
- Power supply for PIN diodes... need 10 mA per diode.

Dual Supply Bus Transceiver

SN74LVC8T245 8-BIT DUAL-SUPPLY BUS TRANSCEIVER WITH CONFIGURABLE VOLTAGE TRANSLATION AND 3-STATE OUTPUTS


SCES584 – JULY 2004

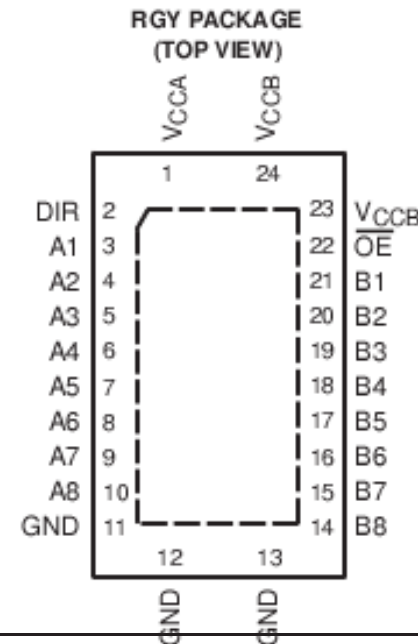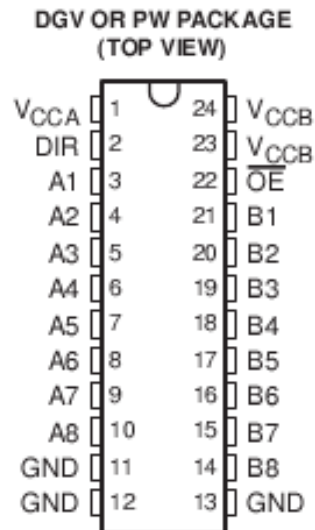- Control Inputs V_{IH}/V_{IL} Levels Are Referenced to V_{CCA} Voltage
- V_{CC} Isolation Feature – If Either V_{CC} Input Is at GND, All I/O Ports Are in the High-Impedance State
- I_{off} Supports Partial-Power-Down Mode Operation
- Fully Configurable Dual-Rail Design Allows Each Port to Operate Over the Full 1.65-V to 5.5-V Power-Supply Range




AD9874 IF Digitising Subsystem

FUNCTIONAL BLOCK DIAGRAM

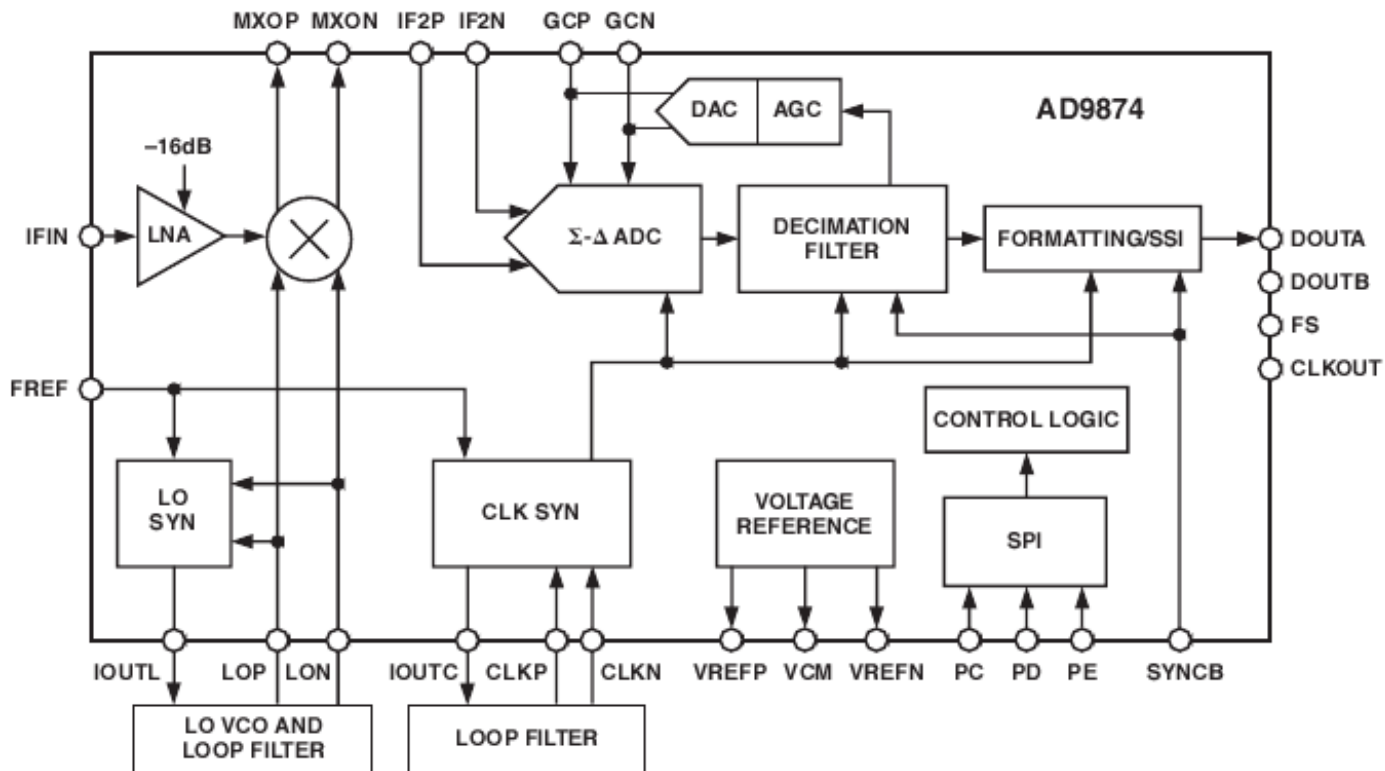

The AD9874 based superhet

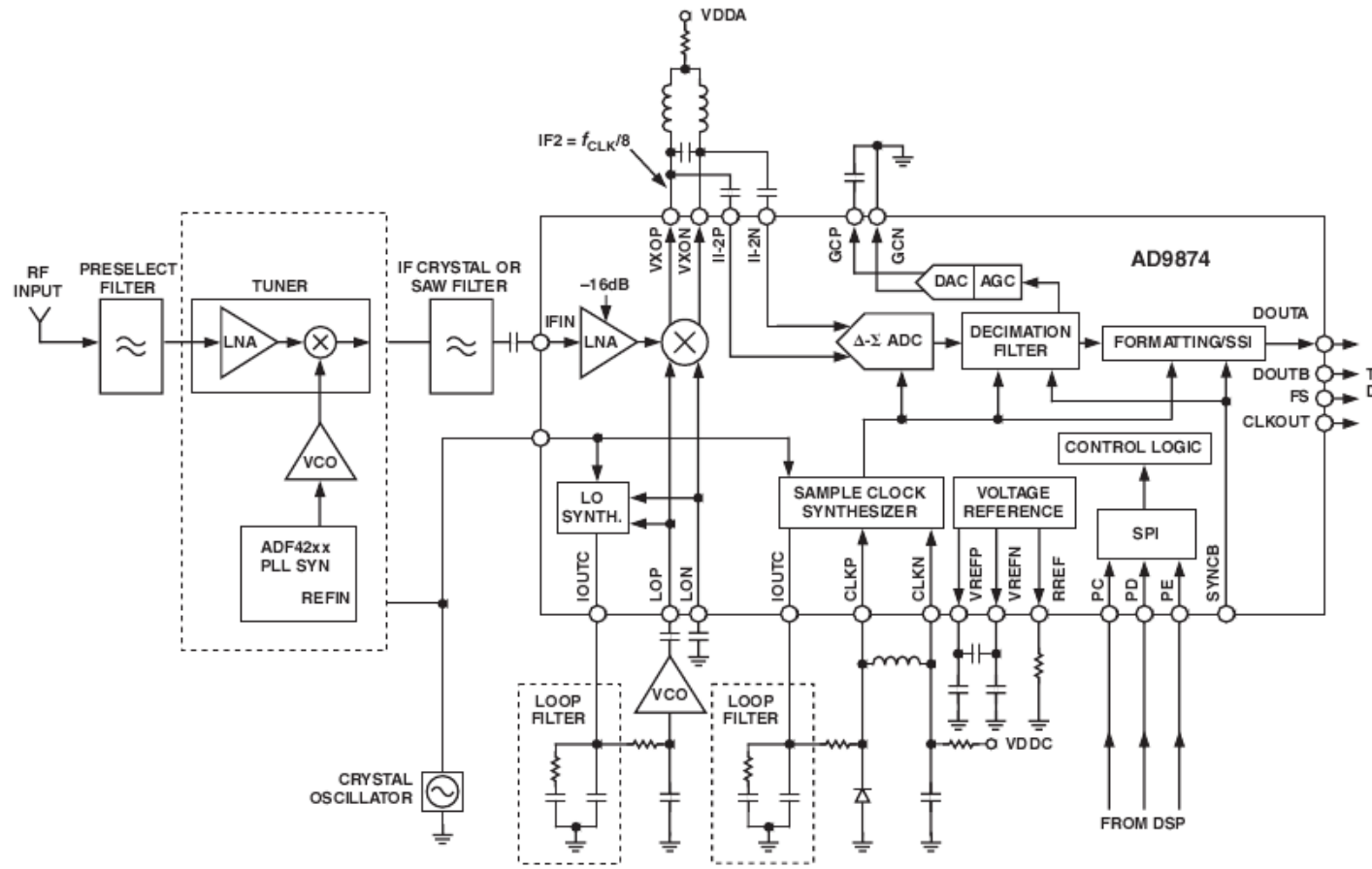

AD9874 Circuit

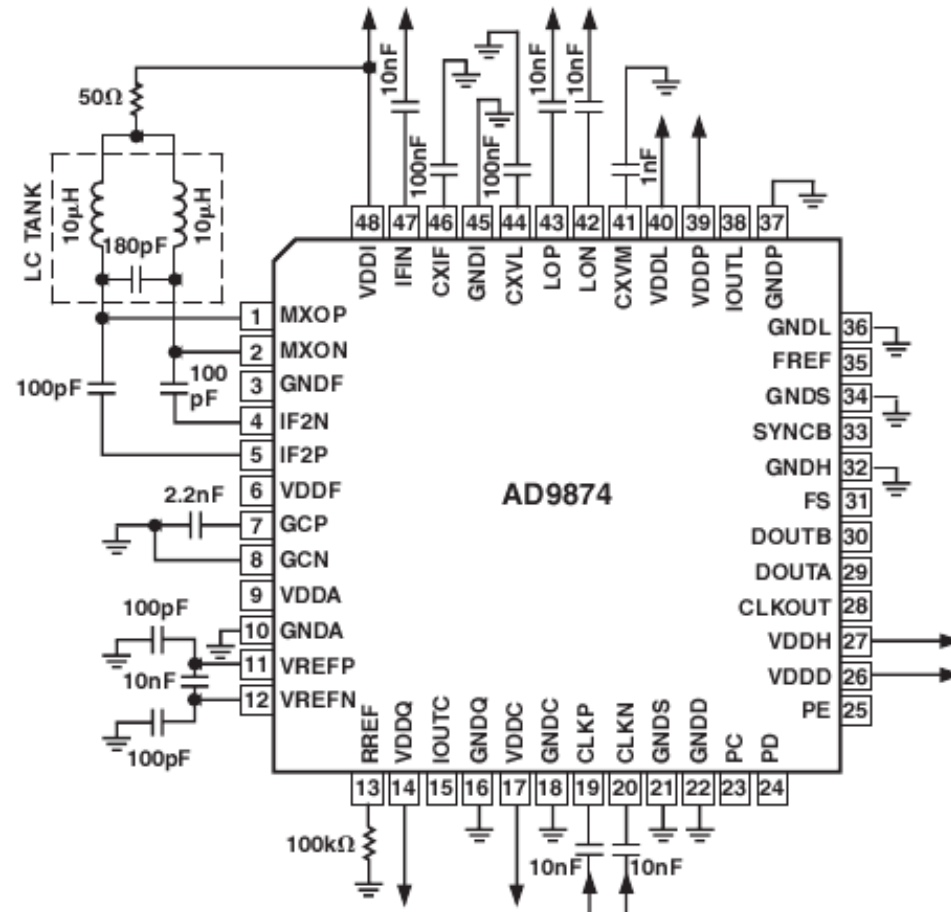


Figure 26. Example Circuit Showing Recommended Component Values