Project ENGN4545

- ► More on transformers: LC resonator filters
- ► Transistors
- ► Transistor S-parameters and Y-parameters
- Transistors and transformers in solve.



LC (Helical) Resonator Filters

- ► Back to back electrostatically coupled transformers.
- Make excellent narrowband filtes.





LC resonator filter design technique

- > We design in the same way as Pi and T matching networks.
- > A semi intuitive design procedure.
- > Divide the circuit into two halves through the coupling capacitor C_c .
- > Consider matching the source (or load) Z_o to a virtual resistance, R'.





LC resonator filter design technique

> Absorb the coupling capacitor C_c into the tuning capacitor C_T .

$$R = R' + \frac{1}{\omega^2 C_c^2 R'} C_c - > \frac{C_c}{1 + (\omega C_c R')^2}$$

> We can now simplify to the following,





LC resonator filters: Things to notice...

- > We now have a matching network which matches Z_o to R.
- The coupling capacitor C_c has been eliminated from the design flow. This means that we will not be able to choose it mathematically. Instead, We choose it *physically* using MATLAB.
- > C_c nonetheless plays an important role in the circuit, for without it, no signal can pass from one side of the circuit to the other.
- It should be clear that for a narrowband filter we are going to design a high Q L-matching network.



LC resonator filter design technique using autotransformer theory

- > We have a matching network to match Z_o to R.
- > We do not know R. Instead we choose Q.
- > Specifying Q is the **only** step in the process!
- ► First we must model the autotransformer.
- Represent the autotransformer as the T-circuit equivalent of inductors...





The Autotransformer

- An autotransformer is a special transformer in which there is only one turn. The "primary" is formed by a tap on the "secondary".
- In an autotransformer $V_1 = \nu V_2$, where V_1 is the primary tap voltage and V_2 is the voltage across the whole transformer. (the secondary!).
- > ν is the ratio of the tap turn number to the total number of turns on the transformer.
- > The mutual inductance, $M = \nu L$, where L is the total inductance of the transformer and $L_1 = \nu^2 L$.



Proof of these relations for the Autotransformer

> The equations of a general transformer are given by,

$$V_1 = j\omega L_1 i_1 + j\omega M i_2$$

$$V_2 = j\omega M i_1 + j\omega L_2 i_2$$

> The autotransformer and its transformer equivalent:

$$i_{1} = V_{2}$$

$$i_{1} = V_{1}$$

$$i_{1} = V_{1}$$

$$i_{1} = V_{1}$$

$$i_{1} = V_{1}$$



Proof of these relations for the Autotransformer

> Multiply the second equation by ν .

 $V_1 = j\omega L_1 i_1 + j\omega M i_2$

$$\nu V_2 = V_1 = j\omega\nu M i_1 + j\omega\nu L_2 i_2$$

- ► If we use $V_1 = \nu V_2$ to replace V_2 , then we have two identical equations in V_1 .
- Equate the coefficients of i_1 and i_2 and we obtain, $L_1 = \nu M$ and $M = \nu L_2$.
- Finally substitute L for L_2 (the total inductance) and then $M = \nu L$ and $L_1 = \nu M = \nu^2 L$. -Q.E.D.



Proof of these relations for the Autotransformer

> We can replace the transformer T-circuit as follows.





Back to the LC resonator

> The LC resonator now has the following simple form,





Back to the LC resonator

- > Can still simplify this.
- > In order to get a high Q circuit, the input impedance of the input to the transformer must be much lower than Z_o , hence

 $Z_o \gg \omega \nu (1-\nu) L$





The LC resonator

Finally express the left leg parallel combination of Z_o and νL as a series combination,





The LC resonator

- Now apply the matching technique for L-type matching networks.
- The only difference is that because we do not know R we must choose Q instead. A very convenient situation!

$$R = \frac{(\omega \nu L)^2}{Z_o} \left(1 + Q^2 \right) \approx \frac{(\omega \nu L Q)^2}{Z_o}$$

provided $Q \gg 1$. And

$$Q = \omega C_T R = \frac{Z_o \omega L}{(\omega \nu L)^2} = \frac{Z_o}{\omega L \nu^2}$$



The LC resonator

If we express the left leg as a parallel rather than a series combination we obtain,

$$R = \frac{Z_o}{\nu^2}$$
 and $\omega^2 L C_T = 1$





The LC resonator design procedure

▶ Guess L. Say
$$L = 1\mu H$$
.

- **>** Compute $C_T = 1/\omega^2/L$
- ► Choose Q.
- **>** Compute ν

$$\nu = \sqrt{\frac{Z_o}{\omega QL}}$$

> ν gives us the tap location, $L_1 = \nu^2 L$, the mutual inductance, $M = \nu L$.

> Also
$$L_2 = L$$
.



Example

- > Design a narrowband filter for 50 MHz.
- ► Let Q = 100 and L=100 nH.
- \blacktriangleright Choose a value of C_c







Consider the following





Divide in half as usual





$$C = \frac{2C_c}{1 + (2\omega C_c R)^2}$$

and

$$R = Z_o \left(1 + Q^2 \right)$$

$$C + C_T = \frac{Q}{\omega R}, \quad and \quad L_T = \frac{QZ_o}{\omega}$$



- > Once again C_c is not in the design flow so we have to guess it while using MATLAB to improve the performance.
- Note that if we change the centre frequency ω to ω/r , then we can scale the circuit components as follows,

$$L_T = rL_T, C_T = rC_T$$
 and $C_c = rC_c$.

► Thus to do a design for a different frequency just change r.

