# **Four Ports**

- Theorems of four port networks
- ▶ 180 ° and 90° Hybrids
- Directional couplers
- > Transmission line transformers, Four port striplines
- ► Rat-races, Wilkinsons, Magic-T's
- Circulators, Diplexers and Filter Diplexers



# **Definition of a Four Port Device**

- Until now transformers and transmission lines have been treated as two port devices.. (deliberate)
- Can also define a 4×4 S-parameter scattering matrix where S<sub>ij</sub> describes the scattered voltage from port i to port j.
- > Four port devices with  $S_{ij} = S_{ji}$  are termed *reciprocal*.





### **Passive vs Active Devices**

A passive device contains no source that adds power to your signal. Conservation of energy, implies that a passive device can't oscillate. The important properties of a passive network are:

> Whether it is reciprocal or non-reciprocal

- Whether it is lossy or lossless. For a four port device insertion loss is due to internal dissipation or resistance in the device.
- > Whether it is impedance matched or unmatched.

Exceptions are *Mixers*. Why?



# **Reciprocal vs Non-Reciprocal Devices**

- A reciprocal network is one in which the power losses are the same between any two ports regardless of direction of propagation (scattering parameter S<sub>ij</sub> = S<sub>ji</sub>).
- A network is known to be reciprocal if it is passive and contains only isotropic materials.
- Examples of reciprocal networks include cables, attenuators, couplers, and antenna systems.



# Non-Reciprocal and Non-Unilateral Devices.

*Anisotopic materials* lead to non-reciprocal devices. Examples of anisotropic media are *magnetised ferrites*, certain *composite and photonic materials* (birefringence) and *magnetised plasmas*.

- An anisotropic material in one in which the values of the relative dielectric constant (and/or relative permeability) depends on the orientation (polarisation) of the electric (and/or magnetic) field vector.
- This implies that waves of different polarisation propagate at different phase speeds.

Other non-reciprocal devices are non-unilateral devices such as transistors.



#### **Three Port Devices**

Theorem: It is impossible for a three-port network to be at the same time reciprocal, lossless and matched.

> You can only have two of these properties at the same time!.





# Proof

The network is matched and lossless so, input 1 Watt into port 1, port 2, port 3 in turn, then

 $1 = |S_{21}|^2 + |S_{31}|^2, \ 1 = |S_{12}|^2 + |S_{32}|^2, \ 1 = |S_{23}|^2 + |S_{13}|^2$ 

- ► Suppose that the network is reciprocal. Then  $S_{21} = S_{12}$ , etc. We conclude that,  $|S_{31}| = |S_{32}|$ ,  $|S_{13}| = |S_{12}|$  and  $|S_{21}| = |S_{23}|$ .
- ► If  $|S_{31}| = |S_{32}|$  then we can send 1 Watt into ports 1 amd 2 but with a phase such that the power emerging from port 3 is zero.
- > Then the power emerging from ports 1 and 2 respectively are  $S_{21}$  and  $S_{12}$ . Power conservation implies that,

$$2 = |S_{21}|^2 + |S_{12}|^2 = 2|S_{21}|^2 < 2$$

because  $|S_{21}|$  is at most unity. It cannot equal unity because from the above  $1 = |S_{21}|^2 + |S_{31}|^2$ , means  $|S_{31}|^2 = 0$ . But  $|S_{13}| = |S_{12}|$ Contradiction!



#### **Three Port Devices: The Circulator**

- An example of a three port device that is both matched and lossless is the The Circulator
- In a circulator, power incident on one port always goes to the right! (or the left)



Figure 1. Symbolic Expression for a Y-Junction Circulator



#### **Fundamentals of Four Port Devices**

There are two fundamental types of lossless, matched and reciprocal four port devices known as 180° and 90° Hybrids





# Fundamental Observations About Four Port Devices





#### **Four Port Devices**

> Put 1 Watt into ports A and B with arbitrary phases  $\phi_{AD}$ ,  $\phi_{AC}$ ,  $\phi_{BC}$  and  $\phi_{BD}$ . Then the output powers can be written,

 $C = 1 + \cos(\phi_{AC} - \phi_{BC}), D = 1 + \cos(\phi_{AD} - \phi_{BD})$ 

From which energy conservation implies,

 $0 = \cos \left(\phi_{AC} - \phi_{BC}\right) + \cos \left(\phi_{AD} - \phi_{BD}\right)$ 

> We distinguish two cases, ( $\phi_{AC} = 0^o$ ,  $\phi_{AD} = 0^o$ ) and ( $\phi_{AC} = 0^o$ ,  $\phi_{AD} = 90^o$ ).



### The 180° and 90° Hybrids





# The 180<sup>o</sup> Hybrid

#### Table 1 - Power Divider Relationships for 180° Hybrids

		Output Signals			
Input Signal	Input Port	Port A	Port B	Port C	Port D
	A	_	0	0.707 E cos(ωt)	
E cos(ωt)	В	0	_	0.707 E cos(ωt)	0.707 E cos(ωt)
	С	0.707 E cos(ωt)	0.707 E cos(ωt)	-	0
	D	0.707 E cos(ωt-180°)	0.707 E cos(ωt)	0	-

This chart assumes only one generator at a time is operating.
Infinite isolation is assumed in the hybrid junction.

3) This is only applicable to RF and Magic T configurations. (Figures 1a and 2) for Microwave frequency Schiffman - type 180° hybrids, use Table 1A.



# The 90° Hybrids



Figure 6. Microwave Frequency 90° Hybrid Schematics and Phase Truth Table



### **Transmission Line Transformers**

- ► One way to make 180<sup>o</sup> Hybrids.
- > Transformers and transmission lines are equivalent at Radiofrequency!





### **Transmission Line Transformer 180**<sup>o</sup> Hybrid





# **The Magic-T**





# **The Magic-T**



